

$V(t)$ in an RC Circuit

